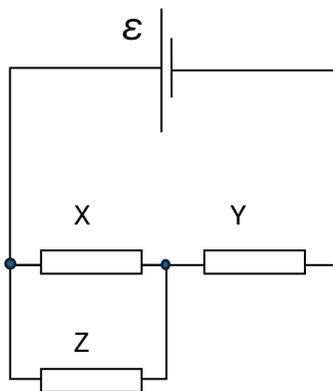


## Teacher notes

### Topic B

#### A question students often get wrong.

Three identical resistors are connected as shown. The cell has no internal resistance.



Resistor Z burns out. What happens to the current in X and the current in Y?

Most students say that the current in Y will stay the same and struggle with the current in X. The claim that the current in Y stays the same stems from the fact that Y gets the current sent out by the cell. But this ignores the fact that when Z burns out the total resistance of the circuit changes and so the current will change.

Here are three approaches with decreasing mathematical machinery.

- (a) The total resistance in the original circuit is  $\frac{R}{2} + R = \frac{3R}{2}$ . Hence the current in the cell is  $I = \frac{\epsilon}{\frac{3R}{2}} = \frac{2\epsilon}{3R}$ . Hence X takes a current  $I_X = \frac{1}{2} \frac{2\epsilon}{3R} = \frac{\epsilon}{3R}$  and Y takes  $I_Y = \frac{2\epsilon}{3R}$ .

When Z burns out the total resistance is  $2R$  and the cell current is  $I = \frac{\epsilon}{2R}$ . This is the new current in both X and Y. So, we see that the current in X increases and that in Y decreases.

- (b) In the original circuit, X has a voltage  $V_X = \frac{\epsilon}{3}$  and Y a voltage  $V_Y = \frac{2\epsilon}{3}$ . With Z burnt out both X and Y have a voltage  $V_X = V_Y = \frac{\epsilon}{2}$ . So, the voltage across X increases and that across Y decreases. Since  $I = \frac{V}{R}$  the current in X will increase and that in Y will decrease.
- (c) With Z burnt out the total resistance increases (we lose the parallel connection) and so the cell current decreases, decreasing the current in Y. This decreases the voltage across Y and so increases the voltage across X. Hence, the current in X will increase.